

## ASSIGNMENT 2

(from Principles of Digital Design Reference Book)

### Chapter 6 – Sequential Logic

**6.16 (Sequential synthesis) Design a counter that counts in the sequence 0, 1, 3, 6, 10, 15 using four (a) D, (b) SR, (c) JK, (d) T flip-flops as memory elements and natural binary encoding.**

Covert these number to binary:

0 = 0000, 1 = 0001, 3 = 0010, 6 = 0110, 10 = 1010, 15 = 1111

a) Using D flipflop:

The truth table:

current state				next sate				output			
Q3	Q2	Q1	Q0	Q3'	Q2'	Q1'	Q0'	D3	D2	D1	D0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	1	0	0	1	1
0	0	1	1	0	1	1	0	0	1	1	0
0	1	1	0	1	0	1	0	1	0	1	0
1	0	1	0	1	1	1	1	1	1	1	1


Karnaugh mapping for D flipflop, we have:

$$D0 = Q0 \text{ xor } 1$$

$$D1 = Q1 \text{ xor } Q0$$

$$D2 = Q2 \text{ xor } (Q1Q0)$$

$$D3 = Q3 \text{ xor } (Q2Q1Q0)$$

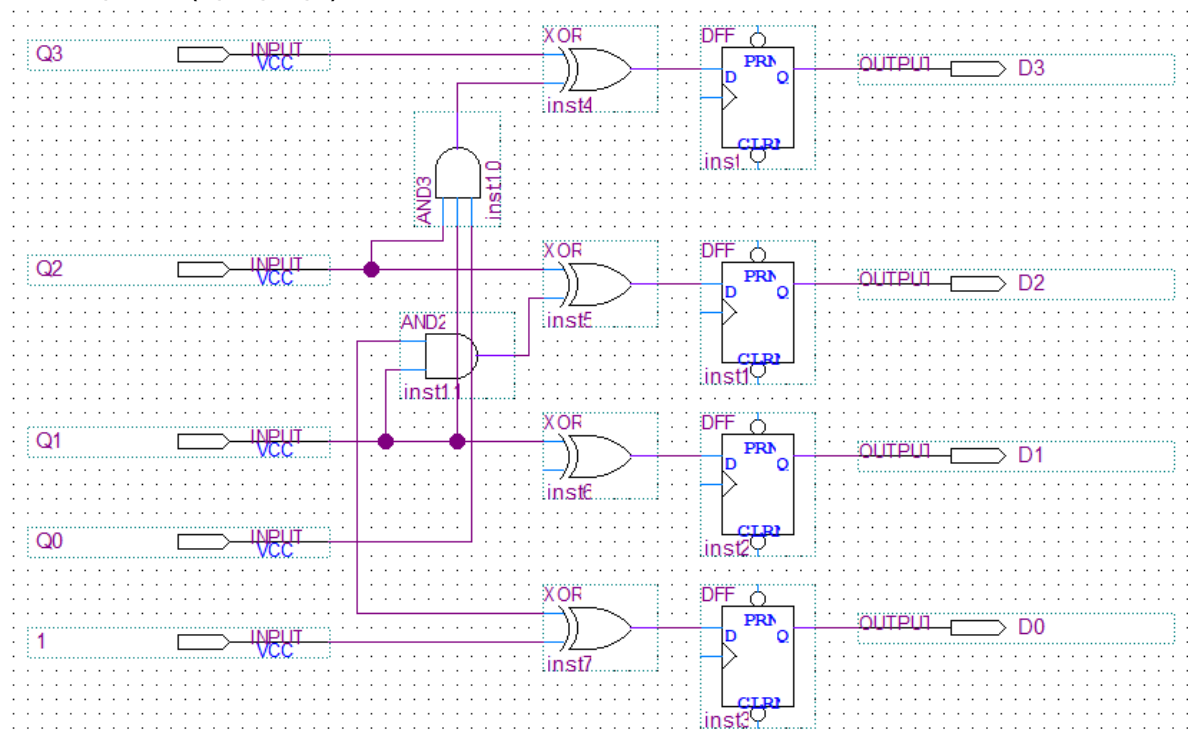

## b) Using SR flipflop:

current state				next state				output							
Q3	Q2	Q1	Q0	Q3'	Q2'	Q1'	Q0'	S3	S2	S1	S0	R3	R2	R1	R0
0	0	0	0	0	0	0	1	0	0	0	1	X	X	X	0
0	0	0	1	0	0	1	1	0	0	1	X	X	X	0	0
0	0	1	1	0	1	1	0	0	1	X	0	X	0	0	1
0	1	1	0	1	0	1	0	1	0	X	0	0	1	0	X
1	0	1	0	1	1	1	1	X	1	X	1	0	0	0	0


Karnaugh mapping for JK flipflop, we have:

$$S0 = Q0', \quad R0 = Q0$$

$$S1 = Q0Q1', \quad R1 = Q0Q1$$

$$S2 = Q2'Q1Q0, \quad R2 = Q2Q1Q0$$

$$S3 = Q3'Q2Q1Q0, \quad R3 = Q3Q2Q1Q0$$

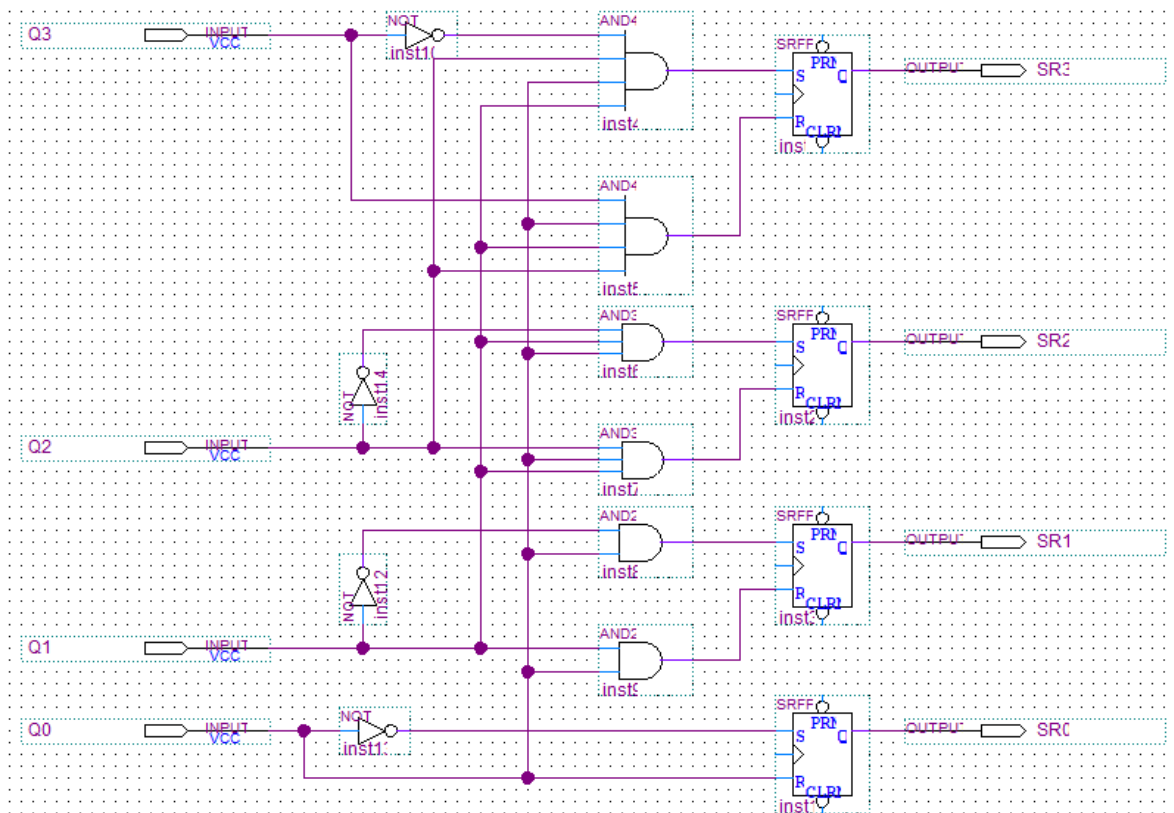

## c) Using JK flipflop:

current state				next state				output							
Q3	Q2	Q1	Q0	Q3'	Q2'	Q1'	Q0'	J3	J2	J1	J0	K3	K2	K1	K0
0	0	0	0	0	0	0	1	0	0	0	1	X	X	X	X
0	0	0	1	0	0	1	1	0	0	1	X	X	X	X	0
0	0	1	1	0	1	1	0	0	1	X	X	X	X	0	1
0	1	1	0	1	0	1	0	1	X	X	0	X	1	0	X
1	0	1	0	1	1	1	1	X	1	X	1	0	X	0	X


Karnaugh mapping for JK flipflop, we have:

$$J0 = K0 = 1$$

$$J1 = K1 = Q1$$

$$J2 = K2 = Q1Q0$$

$$J3 = K3 = Q2Q1Q0$$

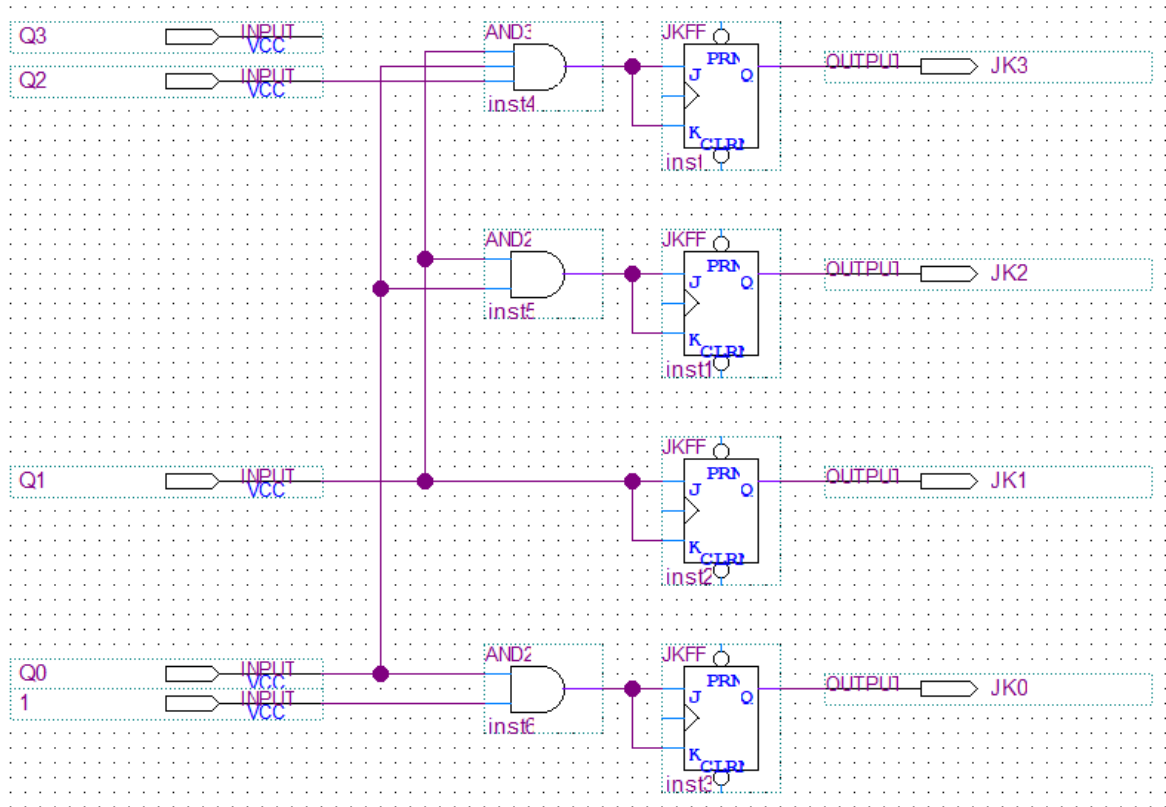

d) Using T flipflop:

current state				next state				output			
Q3	Q2	Q1	Q0	Q3'	Q2'	Q1'	Q0'	T3	T2	T1	T0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	1	0	0	1	0
0	0	1	1	0	1	1	0	0	1	0	1
0	1	1	0	1	0	1	0	1	1	0	0
1	0	1	0	1	1	1	1	0	1	0	1


Karnaugh mapping for T flipflop, we have:

$$T0 = 1$$

$$T1 = Q1$$

$$T2 = Q1Q0$$

$$T3 = Q2Q1Q0$$

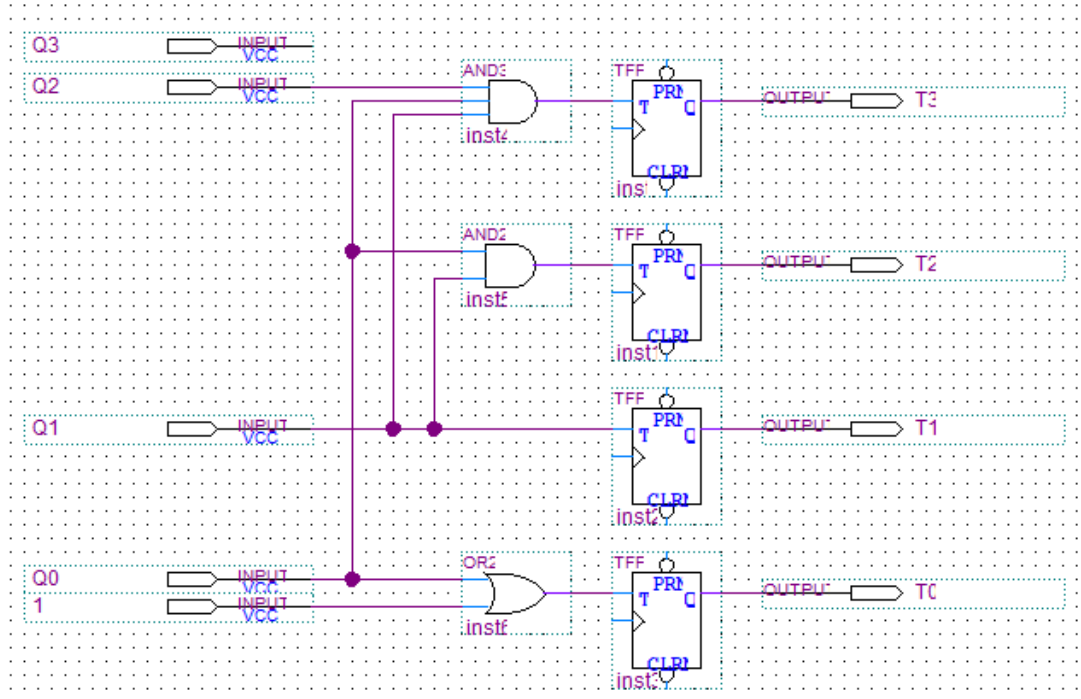


**6.18 (Sequential synthesis) Design a parity checker that counts the number of 1's in the input stream. This checker asserts its output Y if it has received an odd number of 1's on the input X. An asynchronous Reset signal returns the parity checker into its initial state. As storage elements use only (a) D, (b) JK and (c) T flip-flops.**


State transition table:

Current state	Input X	Next state	Output Y
S0	0	S0	0
S0	1	S1	1
S1	0	S1	1
S1	1	S0	0


a) Using D flipflop:

 

b) Using JK flipflop:

 

c) Using T flipflop:

 


**6.19 (Sequential synthesis) Design a recognizer that recognizes an input sequence that has at least three 1's. The recognizer has a single input X and a single output Y, in addition to an asynchronous Reset signal. The recognizer sets the output Y to 1 if the input signal X equals 1 at least three clock cycles after Reset was disasserted. For the recognizer described above:**

- Devise the state diagram.
- Minimize the number of state.
- Encoded the states to minimize the combinatorial logic.
- Draw a schematic diagram using D flip-flop.

Define the state as the following:

- S0: 0 ones received
- S1: 1 ones received
- S2: 2 ones received
- S3: 3 ones received

The state diagram is:

 

Current state	Next state	
	WALK = 0	WALK = 1
S0	S0/0	S1/0
S1	S1/0	S2/0

S2	S2/0	S3/0
S3	S3/1	S3/1

From the state/output table, we can minimize the state number by using implication table:


S3	< S0, S3 > < S3, S2 >		
S2	< S0, S2 > < S3, S3 >	< S3, S2 > < S2, S3 >	
S3			
	S0	S3	S2

The equations defining the implementation can be describe as:

$$D0 = Q0X' + Q1'X$$

$$D1 = Q1 + Q0X$$

$$Y = Q1Q0'$$

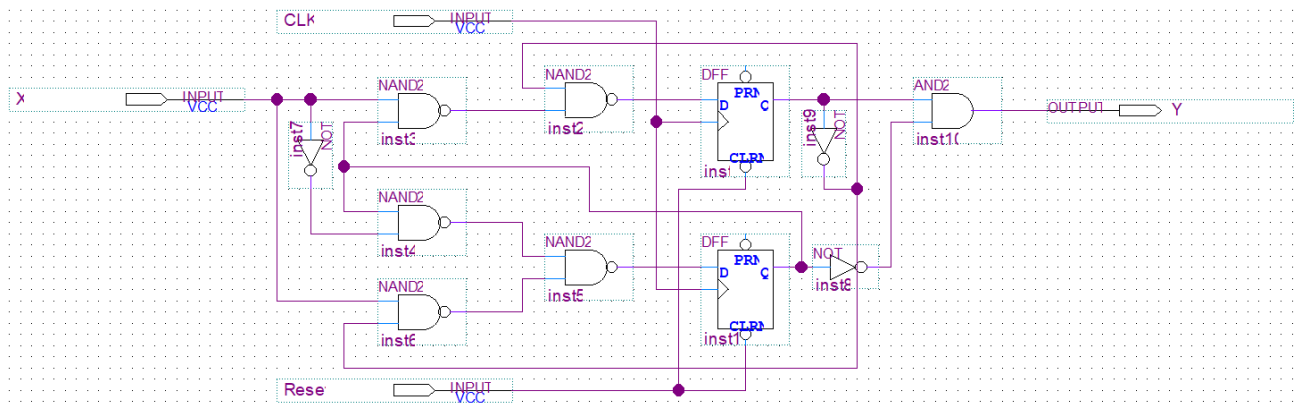

- 6.22 (Sequential synthesis) Design a simplified traffic-light controller that switches traffic lights on a crossing where a north-south (NS) street intersects an east-west (EW) street. The input to the controller is the WALK button pushed by pedestrians who want to cross the street. The outputs are two signals NS and EW that control the traffic lights in the NS and EW directions. When NS or EWW are 0, the red light is on, and when they are 1, the green lights is on. Where there are no pedestrians, NS = 0 and EW = 1 for 1 minute, followed by NS = 1 and EW = 0 for 1 minute, and so on. When a WALK button is pushed, NS and EW both become 1 for a minute when the present minute expires. After that the NS and EW signals continue alternating. For these traffic-light controller:**
- Develop a state diagram and a state/output table.**
  - Minimize the number of states.**
  - Encode the states.**
  - Derive a logic schematic.**


Define the state as the following:

$$S0: NS = 0, EW = 1$$

$$S1: NS = 1, EW = 0$$


$$S2: NS = 1, EW = 1$$

The state diagram is:

 

Current state	Next state	
	WALK = 0	WALK = 1
S0	S1/01	S2/01
S1	S0/10	S2/10
S2	S0/11	S2/11

 As you can see below, the number of state is minimal:



Using minimum-bit change strategy, get the minimizing state encoding as follows:

S0 = 00, S1 = 01, S2 = 10

Current state	Next state	
	WALK = 0	WALK = 1
00	01/01	10/01
01	00/10	10/10
11	XX/XX	XX/XX
10	00/11	10/11

The equations defining the implimentation can be describe as:

$$D0 = Q1'Q0WALK$$

$$D1 = WALK$$

$$NS = Q0 + Q1$$

$$EW = Q0'$$

